
Lab assignment 01 (submit before 12:00 Fri. pm.)

Task 1 (10%): Use a multimeter to measure the resistance of on your table. (4 resistors, set the dial to Ω)

Resitors	R1	R2	R3	R4
Resistance (Ω)				

Task 2 (10%): Use a multimeter to measure the voltage of a 1.5 V battery. Record the measured value. Is it exactly equal to 1.5 V? Then swap two probes, and test the voltage again, record the new value, and explain the result. (set the dial to V)

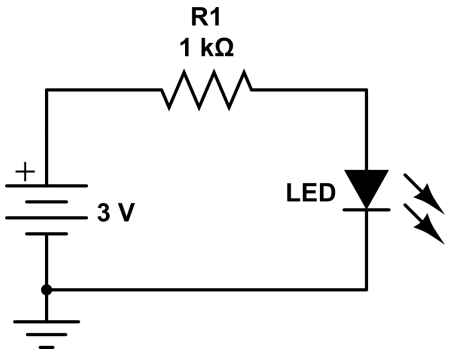
Task 3 (20%): Wire your first circuit on a breadboard to light an LED. Take a picture or your circuit and paste it down below. (Current must enter the LED through the long lead for it to light up)



Task 4 (30%): Wire the following circuit on a breadboard. Take a picture or your circuit and paste it down below. Measure the current and voltage of R1, R2 and R3, and fill the following table. (Set the dial to 

, plug the red lead into 

)

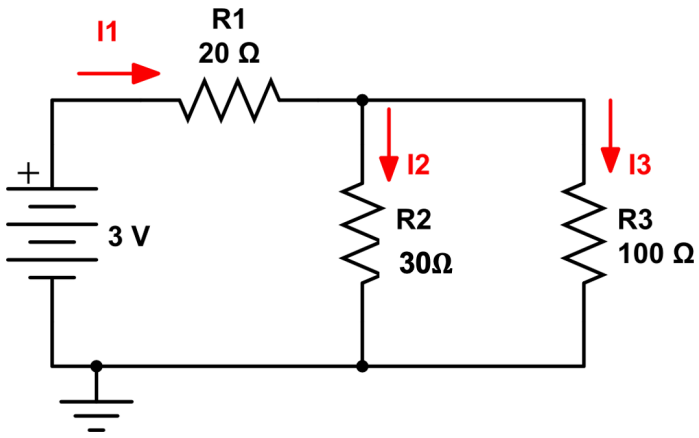

Resistor	R1(20Ω)	R2 (30Ω)	R3 (100Ω)
Current			
Voltage			
Calculated R ($R = v/i$)			

Paste your circuit here:

Task 5(30%): Go to https://www.circuitlab.com/ and sign up with your NYU email. Build the circuit from Task 4, paste it below, and complete the following table.

Component	Battery	R1	R2	R3
Current				
Voltage				
Power				
Absorbing or supplying power?				

Paste your circuit here: